

# Digital Hardware Design Laboratory

## Advanced VHDL and Pipelining

M. Sc. Simon Reder, M. Eng. Augusto Hoppe

### Head of institute

Prof. Dr.-Ing. Dr. h. c. Jürgen Becker

Prof. Dr.-Ing. Eric Sax

Prof. Dr. rer. nat. Wilhelm Stork

Institute for Information Processing Technologies (ITIV)



# VHDL $\leftrightarrow$ Software Coding

## ■ VHDL describes Logic Resources

- Within Process: In Sequence (Process Update...)
- Process-to-Process: In Parallel

## ■ Preferable: **Synchronous Processes**

- Easier implementation, more reliable translation into logic cells during Synthesis

## ■ *Asynchronous Processes:*

- Use as low logic as possible
- Calculations may only depend on **synchronous** input data
- **Use it with extreme care** → high potential of **Simulation/Runtime mismatches**

## ■ On Process dependencies and latency issues...

- Avoid using asynchronous „Handshaking“ or asynchronous inputs to Hard-IPs like BRAMs, DSP Slices etc.
- Solve these issues using ***Pipelining***


# VHDL $\leftrightarrow$ Software Coding

- Many operations known from C-programming **cannot or not efficiently** be implemented in Hardware Logic
  - **Delays** using given time values in seconds: „a <= b after 30ns;“
  - **Wait statements** – „wait until“ in modules for Synthesis is bad coding style
  - **Large storages** without using Hard-IPs (BRAMs):
    - „type my\_array is array (natural range <>) of std\_logic vector(31 downto 0);“  
„signal array : my\_array (1023 downto 0);“
  - **Multiplication or Division**
    - by **non-power-of-two** values  $\rightarrow$  long asynchronous logic paths
    - Division/Multiplication **within one Clock-Cycle**, like „c <= a / b;“
    - *Exception:* with DSP Slices c <= a\*b for certain input sizes (amount is very limited on-chip) is possible but still a **very expensive operation**, thinking hardware-wise


# Pipelining in VHDL

- Reduces length of asynchronous paths → increases clock frequency
- Solves issues like:
  - Handshakes between processes requiring low latencies
  - Operations which cannot be performed within one clock cycle (→ e.g. Division)
- Assists in compensating for ***different delays of processing Blocks***

## Implementation with issues

 

## Solution

 

# Pipelining in VHDL

## ■ Description of Delay line in VHDL (Shift register):

- Within Process: **For** loops

...

```
constant delay_const : integer := 8;
signal input_delayed : input_type(delay_const-1 downto 0);
```

begin

```
process(clk, rstn, en)
```

```
begin
```

```
if rstn = '0' then
```

```
input_delayed <= (others => '0');
```

```
elsif rising_edge(clk) then
```

```
input_delayed(delay_const-1) <= input;
```


```
for i in delay_const-2 downto 0 loop
```

```
input_delayed(i) <= input_delayed(i+1);
```

```
end loop;
```

```
output <= input_delayed(0);
```

...

 

# Pipelining in VHDL

## ■ Similar to for loops: **Generate** statement

- Good for implementing regular structures with common properties, e.g. adder trees or in general for structural modelling.

```

Input_registering: process(clk)
begin
  if rising_edge(clk) then
    if rst = '1' then
      stg_0_reg <= (others => (others => '0'));
      stg_1_reg <= (others => (others => '0'));
      stg_2_reg <= (others => (others => '0'));
    else
      for i in 0 to 3 loop
        stg_0_reg(i) <= stg_0(i);
      end loop;

      for i in 1 to 0 loop
        stg_1_reg(i) <= stg_1(i);
      end loop;

      stg_2_reg <= stg_2;
    end if;
  end if;
end process;

```


```

G0: for i in 0 to 3 generate
  stg_0(i) <= input(2*i) + input(2*i + 1);
end generate;

G0: for i in 0 to 1 generate
  stg_1(i) <= stg_0_reg(2*i) + stg_0_reg(2*i + 1);
end generate;

stg_2 <= stg_1_reg(0) + stg_1_reg(1);

```

 

**Example**  
(4 values)

# Arithmetics in VHDL

- For arithmetic operations, the **size of the vector** (e.g. signed) of the **result** is usually of different size than the *input* vectors (here: **VS = vector size**)
- Following rules apply for **UNKNOWN** values of a and b, for not losing information or to avoid values exceeding the vector size.
- **Addition / Subtraction** ( $c = a + b$ ):  **$VS(c) = \max(VS(a), VS(b)) + 1$**
- **Multiplication** ( $c = a * b$ ):  **$VS(c) = VS(a) + VS(b)$**
- *Simplifications may be possible:*  
If e.g. value b is known to be **< const\_val**, then for  **$c = a * b$**  the vector size c may be chosen to  **$VS(c) = VS(a) + \log_2(\text{const\_val})$**

# Polynomial binary division

- Division  $29 / 5 = 5$ , Remainder 4
- Binary Division (*standard procedure*)

$$\begin{array}{r} 011101 \text{ / } 101 = 0101, \text{ Remainder } 100 \\ \underline{011} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \\ - \phantom{0} 0 \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \\ \hline 0111 \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \\ - \phantom{0} \underline{101} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \\ \hline 0100 \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \\ - \phantom{0} 0 \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \\ \hline 1001 \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \phantom{00} \\ - \phantom{0} \phantom{0} \phantom{0} \phantom{0} \underline{101} \phantom{00} \\ \hline 100 \end{array}$$




→ **Efficient Hardware Implementation?**


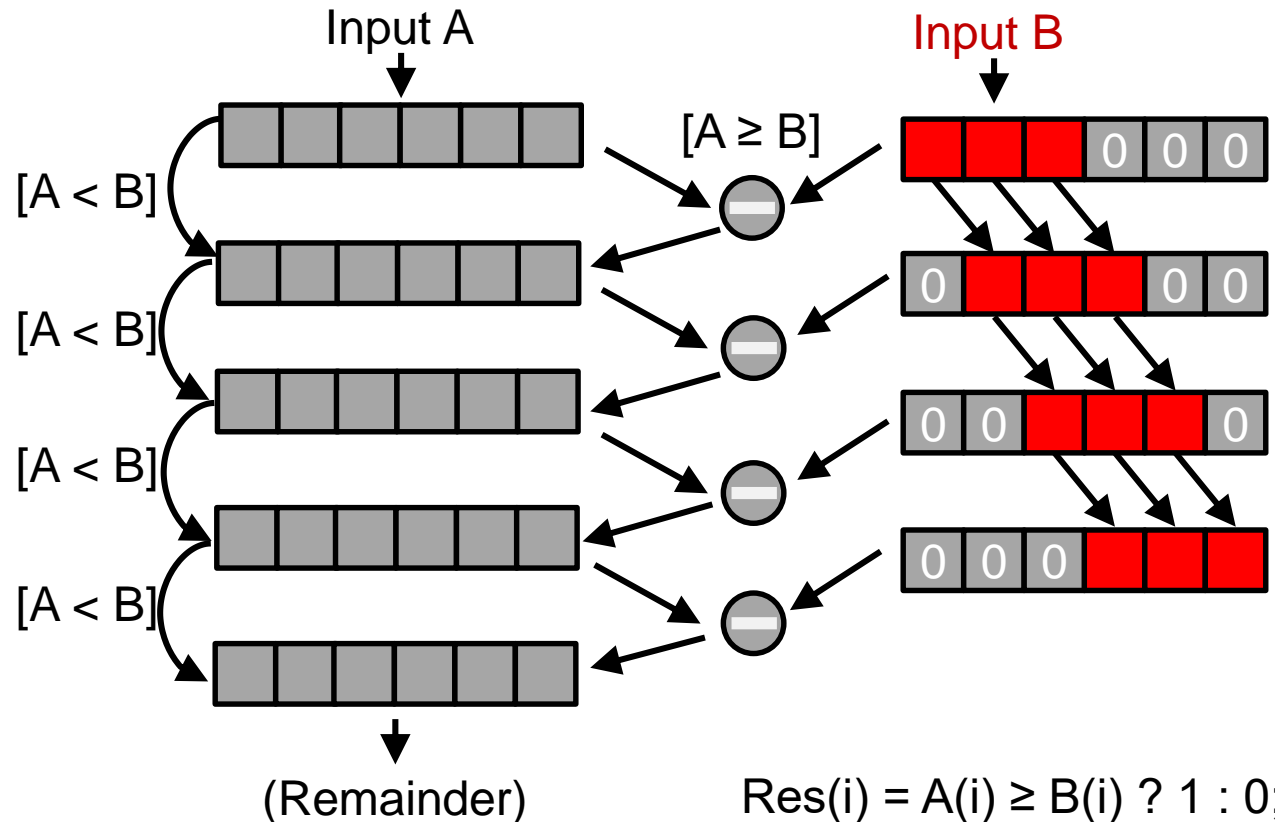
# Polynomial binary division

- Division  $29 / 5 = 5$ , Remainder 4
- Binary Division (implementation with **shift registers**)

$$\begin{array}{r}
 011101 \text{ / } 101 = 0101, \text{ Remainder } 100 \\
 \underline{011101} \\
 - (101000) \\
 \hline
 0 \\
 011101 \\
 - \underline{010100} \\
 01001 \\
 - (01010) \\
 \hline
 0 \\
 01001 \\
 - \underline{0101} \\
 100
 \end{array}$$



# Additional Tutorials/Videos on the Web

Interesting Tutorial Videos:

<http://www.googoolia.com/wp/category/zynq-training/page/2/>

Digilent learning platform:

<https://learn.digilentinc.com/list?category=Digital>

e.g.

- **Zynq Hardware Architecture Highlights**
- **Zynq Development Tools Overview**
- **AXI Bus Overview**
- **HDL Tutorials**
- ...

**Not required  
for examination!**